
Simple SRAM Buffering for Large LED Arrays

<p><i>Author: Tim Friend</i> <i>Microchip Technology Inc.</i></p>

INTRODUCTION

The Configurable Logic Cell (CLC) in the PIC16F1509 microcontroller allows multiple peripherals to be connected together in unique and flexible ways, enabling the creation of custom peripherals that would otherwise be very difficult or would require external logic.

While this application note was written specifically for PIC16F1509, nearly any device with at least two CLC modules will work as well. At the time of this writing, this includes the following PIC® microcontrollers:

- PIC16F1508
- PIC16F1509
- PIC16F1615
- PIC16F1619
- PIC16F1704
- PIC16F1705
- PIC16F1708
- PIC16F1709
- PIC16F1713
- PIC16F1716
- PIC16F1717
- PIC16F1718
- PIC16F1719

Application notes are available which demonstrate extended resolution PWMs, Manchester decoding, glitch suppression and other combinations, without requiring external hardware or “bit-banging”, which refers to toggling an I/O pin in software with (hopefully) the correct timing.

One such application note is AN1606, “*Using the Configurable Logic Cell (CLC) to Interface a PIC16F1509 and WS2811 LED Driver*” (DS00001606), which describes a method of using the Configurable Logic Cell (CLC) to create a custom interface to a series of WS2811/WS2812 LEDs. These LEDs are well-known in LED video display systems and in strip lights with individually addressable LEDs. Each LED allows for 256 levels of brightness on each of the RGB colors, which requires 24 bits, or three bytes of information for each LED in the string. Individual LEDs

are connected serially in a daisy chain format, allowing a single I/O pin to address several, dozens or even hundreds of LEDs.

Because of the strict timing requirements of the serial protocol used by WS2811/WS2812, there is very little time between bytes to compute color information for subsequent LEDs in the string. Once the transmission of data to the LED strings has begun, any gaps in the data will cause the data to be latched into whatever LEDs the data is passing through at that time, resulting in incorrectly displayed information. The usual alternative is to buffer the contents of the LED array in RAM and shift it out in one continuous stream.

For smaller microcontrollers driving larger arrays of LEDs, this buffering of data can rapidly consume all available RAM. This application note describes a method of using the CLC to connect an external serial SRAM as a display buffer, which allows large LED arrays to be driven by smaller microcontrollers.

CUSTOM PERIPHERAL

AN1606 describes the creation of a custom peripheral which uses the CLC to combine the MSSP and a PWM to create the necessary serial protocol for WS2811-WS2812. Please refer to AN1606, for a complete description of this method. AN1606 describes the use of the Low-Speed mode of the WS2811, while what is described in this application note will use the High-Speed mode of WS2811, which is also compatible with WS2812.

A SIMPLE SRAM BUFFER

The CLC configuration described in AN1606 allows WS2811/WS2812 to be driven by simply writing bytes to the SPI port in software. Since the CLC and its combination of peripherals take care of all the protocol timing, the only thing that the software needs to do is keep writing the SPI port until the entire LED array has been updated. The 23LC512 Serial SRAM is connected to the same SPI port and can be used as a display buffer. Since WS2811/WS2812 is a “write only” device, it is possible to read the SRAM and write the LED display simultaneously on the SPI port.

The SPI port on PIC16F1509 implements two Shift registers which exist at the same address, one for transmitting and one for receiving. Writes to the SSP1BUF register will transmit the byte just written and will shift in a byte from the external peripheral at the same time, which then becomes available by reading the SSP1BUF register. By having both the SRAM and the LEDs connected to the SPI port, the software simply needs to read the SSP1BUF register and write the data to the same register to re-transmit it to the LED array. It does this repeatedly until the entire LED array has been updated. The only thing to remember is that a dummy byte has to be written before the display is enabled to allow the first byte from the SRAM buffer to arrive in the SSP1BUF register.

Dealing with potential conflicts between the LEDs and the SRAM being connected to the same SPI port is simply a matter of enabling and disabling the appropriate peripherals. When the SRAM is being written, the output to the LEDs is disabled by reconfiguring the CLC to disable its output. When sending buffered data to the LEDs from the SRAM, the LED output is disabled while the appropriate command byte and address are transmitted to the SRAM. After a dummy byte is transmitted to begin the whole process, the LED output is enabled and software just executes a tight loop, copying the SSP1BUF register to itself whenever an SPI transaction completes. If the software needs to write non-buffered data to the array, such as when writing all zeros (clearing the array), it will not activate the Chip Select to the SRAM.

Depending on how often the LED array needs to be updated, the number of LEDs driven can be arbitrarily large, as the LED array size is limited only by the update rate and the size of the external SRAM. The display buffer can be changed when the display is not being updated, which allows time to do more complex computations, table look-ups and whatever else is needed to build the displayed image.


Having a buffered image in SRAM also allows displayed patterns or images to move by simply using a different starting address in SRAM when updating the LED array. Each iteration of the display update uses a slightly different address offset which will cause the entire displayed image to move.

WS2812 PROTOCOL

The WS2812 serial protocol is PWM-based, with one PWM period being one bit time, and the duty cycle during that period indicating a logic one or a logic zero. The WS2812 PWM period is 1.25 μ s (± 600 ns). A logic zero is represented by a high time of 350 ns and a low time of 800 ns, while a logic one is represented by a high time of 700 ns and a low time of 600 ns. All these times are ± 150 ns. In addition to these two logic states, a third state is defined: a low time greater than 50 μ s represents a Reset, and the WS2812 will latch the current data to its LED drivers when this state is detected. Testing has demonstrated that actual Reset times hover around 6 μ s, so there is very little time for processing between transmitted bytes.


AN1606 describes the SPI signals SCK and SDO ANDed together to generate the logic '1' portion of the LED data, and using a PWM to generate the logic '0' portion of the LED data, and ORing these two together for the desired waveform (see [Figure 1](#)).

FIGURE 1: FINAL WAVEFORMS

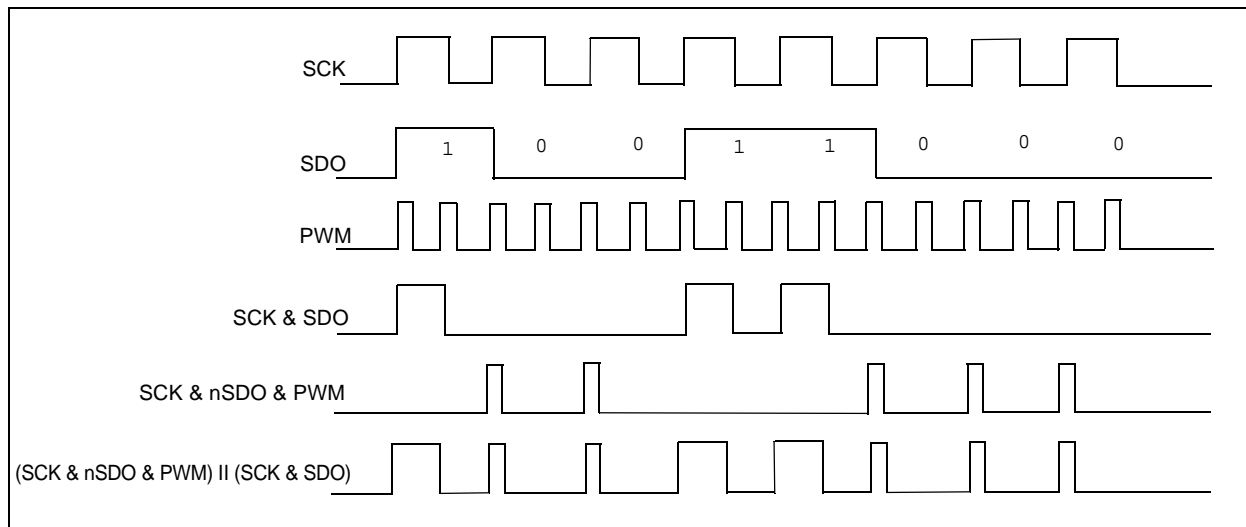

The CLC Designer tool (www.microchip.com/clc) can be used to convert this to the code for the PIC16F1509 microcontroller. For this application, CLC4 was used because of its access to the SPI signals. CLC4 can be set up as shown in Figure 2 below.

FIGURE 2: CLC4 SETUP USING CLC DESIGNER

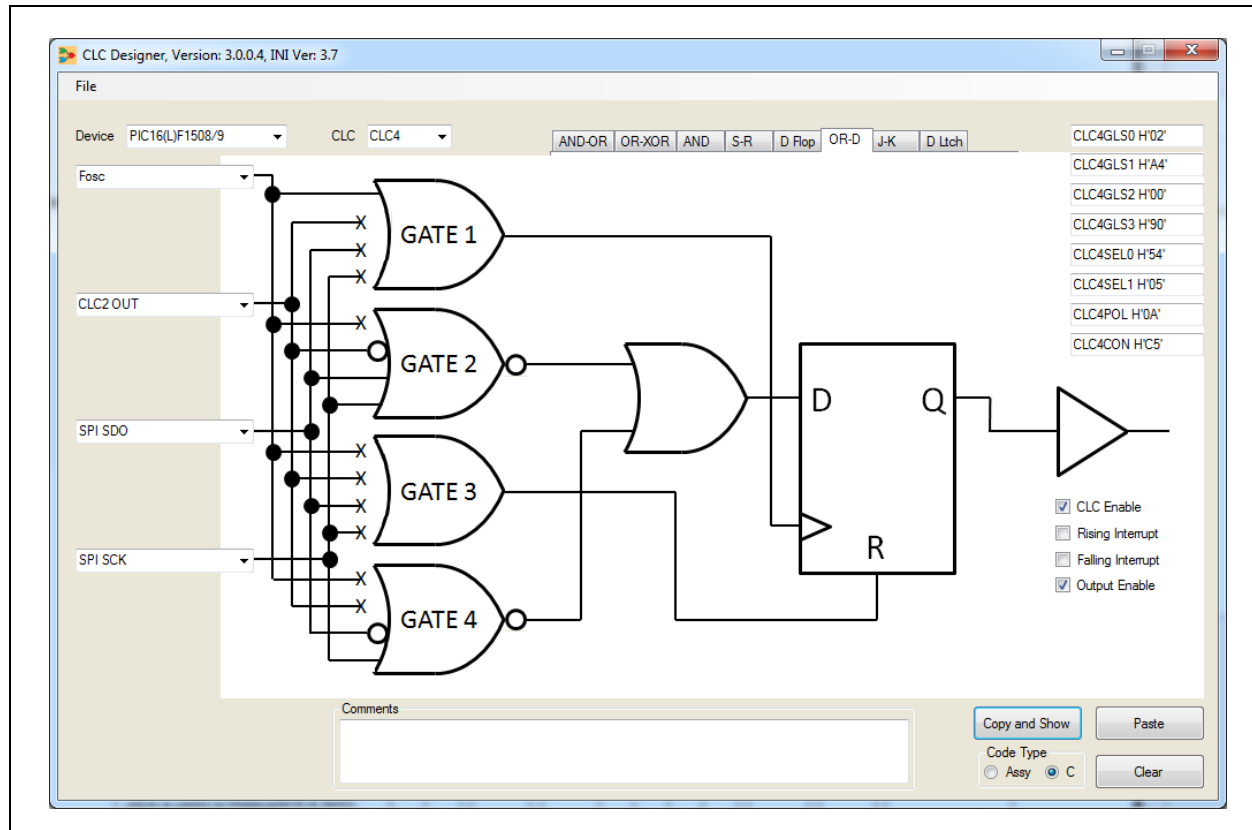

The OR-D configuration was chosen to allow the signals to be resynchronized to the FOSC clock. Although it would probably work without it, this results in more predictable timing at the output. This configuration is displayed as OR-OR, so a little bit of logic conversion is needed to make the original logic equation fit (see Equation 1).

EQUATION 1: ORIGINAL LOGIC FROM AN1606

$$(SCK \& nSDO \& PWM) // (SCK \& SDO)$$

By applying DeMorgan's Theorem, the original equation can be converted to fit the above configuration as seen in Equation 2.

EQUATION 2: APPLICATION OF DEMORGAN'S THEOREM

$$n(nSCK // SDO // nPWM) // n(nSCK // nSDO)$$

This handily fits into gates two and four of CLC4.

Note that CLC2OUT is used for PWM1, since PWM1 is not available at this logic cell. PWM1 is simply routed through another logic cell (CLC2).

When connecting the 23LC512 Serial SRAM, the SRAM needs to be driven by an inverted SPI clock. This is taken into account by one more modification of the Equation 2, which re-inverts the SPI clock, since it needs to be non-inverted in this logic cell. The final equation will look as shown in Equation 3.

EQUATION 3: FINAL LOGIC FOR CLC4


$$n(SCK // SDO // nPWM) // n(SCK // nSDO)$$

This equation is illustrated in the CLC Designer in Figure 2.

IMPLEMENTATION

The connections for a PIC16F1509 are shown in [Figure 3](#) below.

FIGURE 3: SRAM AND LED CONNECTIONS TO THE PIC16F1509

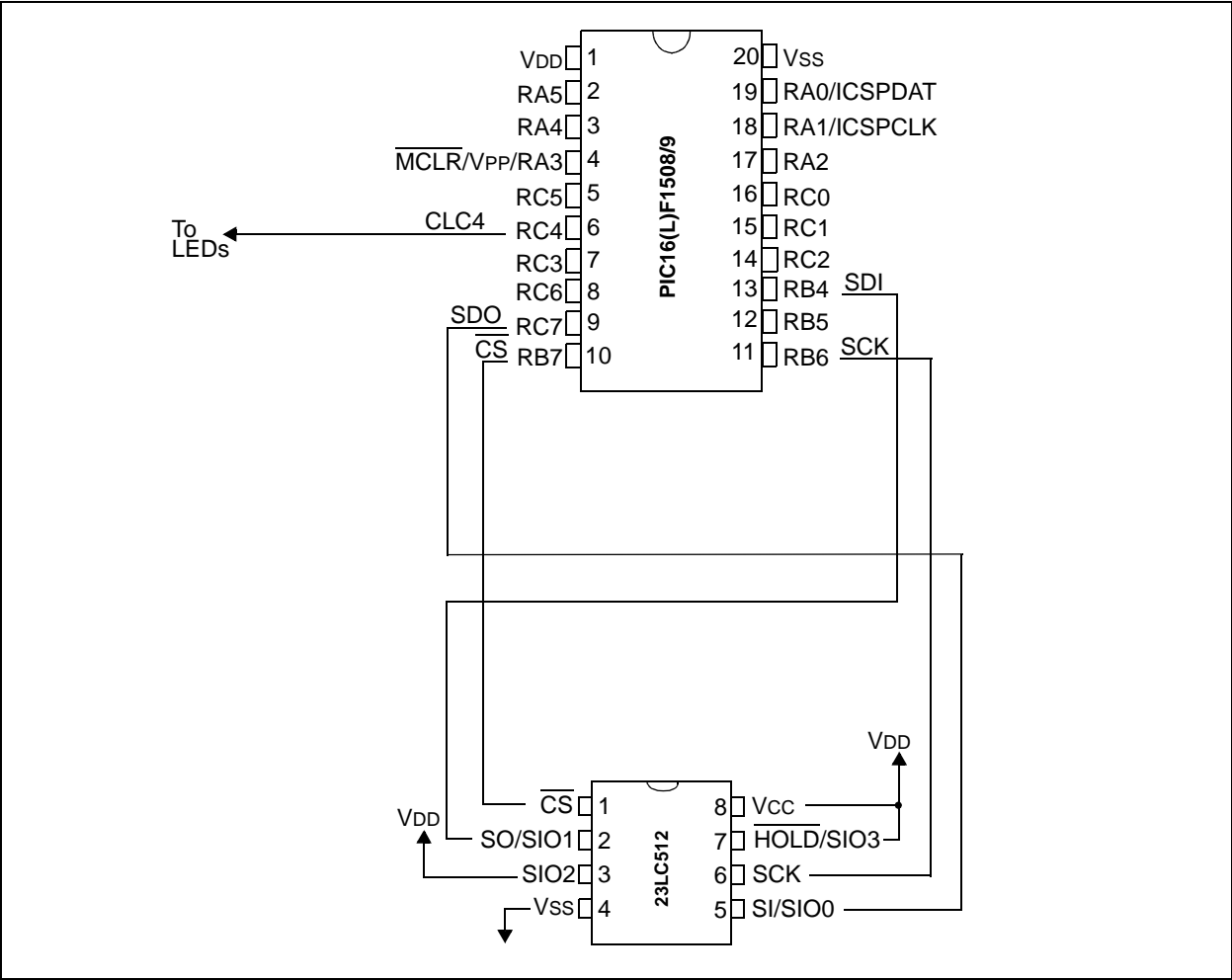

The accompanying source code sets the microcontroller to run at 16 MHz, and all the timing is based on this clock rate.

Timer2 is used as a clock source for the SPI port and also as a timebase for PWM1. If a bit time of 1.25 μ s and a 16 MHz internal oscillator are used, then Timer2 should be set up as shown in [Example 1](#) below.

EXAMPLE 1: TIMER2 SETUP

```
T2CON = 0x04
PR2 = (bit time/2) * (Fosc/4) + 1
```

Plugging in a bit time of 1.25 μ s yields a PR2 value of 2.25. Truncating this to two and using it results in an actual bit time of 1.5 μ s, which is well within the ± 600 ns specification for WS2811/WS2812. Therefore, the obtained value is the one displayed in [Example 2](#).

EXAMPLE 2: PR2 REGISTER VALUE

```
PR2 = 2
```

The PWM duty cycle must be configured for the logic zero-pulse width. This width is specified at 350 ns, so the closest match in terms of 16 MHz clock periods will be chosen. Six clock periods figure out to 375 ns (which is within the specified ± 150 ns), so the logic zero-pulse width needs to be six FOSC cycles wide. The Period register for PWM1 is actually composed of two registers: the High 8-bit register and the Low 2-bit register. The two bits are at the Most Significant end of the PWM1DCL register, so these two registers become as per [Example 3](#).

EXAMPLE 3: PWM1 SETUP

```
PWM1DCH = 1
PWM1DCL = 0x80
```

Configuring the SPI port to use Timer2 Period/2 as the clock and outputting an inverted clock will yield the result indicated in [Example 4](#).

EXAMPLE 4: SPI CONTROL REGISTER SETUP

<code>SSP1CON1 = 0x33</code>

All these are set up in an initialization function in the source code. The source code writes a pattern to the serial SRAM, then sends this pattern to the LEDs periodically, offsetting the SRAM address by three bytes each time, thus causing the pattern to move across a string of LEDs. This demo code was written to drive a string of 60 WS2812 LEDs, but it can be easily modified to drive nearly any number of LEDs, limited only by update rate and available SRAM. The AN1890 source code can be downloaded from the Microchip web site at www.microchip.com/applicationnotes.

CONCLUSION

The CLC enables features that would normally be difficult to do. With just a few lines of code and an external serial SRAM, a small microcontroller like the PIC16F1509 can easily drive an arbitrarily large array of WS2811/WS2812 LEDs with complex patterns. The source code is written entirely in C and is not timing critical, other than keeping the SPI port serviced. This method can be easily modified to fit other microcontrollers containing the CLC peripheral, and the serial SRAM could also be replaced with a serial EEPROM for nonvolatile LED images.

Note the following details of the code protection feature on Microchip devices:

- Microchip products meet the specification contained in their particular Microchip Data Sheet.
- Microchip believes that its family of products is one of the most secure families of its kind on the market today, when used in the intended manner and under normal conditions.
- There are dishonest and possibly illegal methods used to breach the code protection feature. All of these methods, to our knowledge, require using the Microchip products in a manner outside the operating specifications contained in Microchip's Data Sheets. Most likely, the person doing so is engaged in theft of intellectual property.
- Microchip is willing to work with the customer who is concerned about the integrity of their code.
- Neither Microchip nor any other semiconductor manufacturer can guarantee the security of their code. Code protection does not mean that we are guaranteeing the product as "unbreakable."

Code protection is constantly evolving. We at Microchip are committed to continuously improving the code protection features of our products. Attempts to break Microchip's code protection feature may be a violation of the Digital Millennium Copyright Act. If such acts allow unauthorized access to your software or other copyrighted work, you may have a right to sue for relief under that Act.

Information contained in this publication regarding device applications and the like is provided only for your convenience and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. MICROCHIP MAKES NO REPRESENTATIONS OR WARRANTIES OF ANY KIND WHETHER EXPRESS OR IMPLIED, WRITTEN OR ORAL, STATUTORY OR OTHERWISE, RELATED TO THE INFORMATION, INCLUDING BUT NOT LIMITED TO ITS CONDITION, QUALITY, PERFORMANCE, MERCHANTABILITY OR FITNESS FOR PURPOSE. Microchip disclaims all liability arising from this information and its use. Use of Microchip devices in life support and/or safety applications is entirely at the buyer's risk, and the buyer agrees to defend, indemnify and hold harmless Microchip from any and all damages, claims, suits, or expenses resulting from such use. No licenses are conveyed, implicitly or otherwise, under any Microchip intellectual property rights.

Trademarks

The Microchip name and logo, the Microchip logo, dsPIC, FlashFlex, flexPWR, JukeBlox, KEELOQ, KEELOQ logo, Klear, LANCheck, MediaLB, MOST, MOST logo, MPLAB, OptoLyzer, PIC, PICSTART, PIC³² logo, RightTouch, SpyNIC, SST, SST Logo, SuperFlash and UNI/O are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

The Embedded Control Solutions Company and mTouch are registered trademarks of Microchip Technology Incorporated in the U.S.A.

Analog-for-the-Digital Age, BodyCom, chipKIT, chipKIT logo, CodeGuard, dsPICDEM, dsPICDEM.net, ECAN, In-Circuit Serial Programming, ICSP, Inter-Chip Connectivity, KlearNet, KlearNet logo, MiWi, MPASM, MPF, MPLAB Certified logo, MPLIB, MPLINK, MultiTRAK, NetDetach, Omniscient Code Generation, PICDEM, PICDEM.net, PICkit, PICtail, RightTouch logo, REAL ICE, SQI, Serial Quad I/O, Total Endurance, TSHARC, USBCheck, VariSense, ViewSpan, WiperLock, Wireless DNA, and ZENA are trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

SQTP is a service mark of Microchip Technology Incorporated in the U.S.A.

Silicon Storage Technology is a registered trademark of Microchip Technology Inc. in other countries.

GestIC is a registered trademarks of Microchip Technology Germany II GmbH & Co. KG, a subsidiary of Microchip Technology Inc., in other countries.

All other trademarks mentioned herein are property of their respective companies.

© 2015, Microchip Technology Incorporated, Printed in the U.S.A., All Rights Reserved.

ISBN: 978-1-63277-124-7

QUALITY MANAGEMENT SYSTEM
CERTIFIED BY DNV
= ISO/TS 16949 =

Microchip received ISO/TS-16949:2009 certification for its worldwide headquarters, design and wafer fabrication facilities in Chandler and Tempe, Arizona; Gresham, Oregon and design centers in California and India. The Company's quality system processes and procedures are for its PIC® MCUs and dsPIC® DSCs, KEELOQ® code hopping devices, Serial EEPROMs, microperipherals, nonvolatile memory and analog products. In addition, Microchip's quality system for the design and manufacture of development systems is ISO 9001:2000 certified.



Worldwide Sales and Service

AMERICAS

Corporate Office
2355 West Chandler Blvd.
Chandler, AZ 85224-6199
Tel: 480-792-7200
Fax: 480-792-7277
Technical Support:
<http://www.microchip.com/support>
Web Address:
www.microchip.com

Atlanta
Duluth, GA
Tel: 678-957-9614
Fax: 678-957-1455

Austin, TX
Tel: 512-257-3370

Boston
Westborough, MA
Tel: 774-760-0087
Fax: 774-760-0088

Chicago
Itasca, IL
Tel: 630-285-0071
Fax: 630-285-0075

Cleveland
Independence, OH
Tel: 216-447-0464
Fax: 216-447-0643

Dallas
Addison, TX
Tel: 972-818-7423
Fax: 972-818-2924

Detroit
Novi, MI
Tel: 248-848-4000

Houston, TX
Tel: 281-894-5983

Indianapolis
Noblesville, IN
Tel: 317-773-8323
Fax: 317-773-5453

Los Angeles
Mission Viejo, CA
Tel: 949-462-9523
Fax: 949-462-9608

New York, NY
Tel: 631-435-6000

San Jose, CA
Tel: 408-735-9110

Canada - Toronto
Tel: 905-673-0699
Fax: 905-673-6509

ASIA/PACIFIC

Asia Pacific Office
Suites 3707-14, 37th Floor
Tower 6, The Gateway
Harbour City, Kowloon
Hong Kong
Tel: 852-2943-5100
Fax: 852-2401-3431

Australia - Sydney
Tel: 61-2-9868-6733
Fax: 61-2-9868-6755

China - Beijing
Tel: 86-10-8569-7000
Fax: 86-10-8528-2104

China - Chengdu
Tel: 86-28-8665-5511
Fax: 86-28-8665-7889

China - Chongqing
Tel: 86-23-8980-9588
Fax: 86-23-8980-9500

China - Dongguan
Tel: 86-769-8702-9880

China - Hangzhou
Tel: 86-571-8792-8115
Fax: 86-571-8792-8116

China - Hong Kong SAR
Tel: 852-2943-5100
Fax: 852-2401-3431

China - Nanjing
Tel: 86-25-8473-2460
Fax: 86-25-8473-2470

China - Qingdao
Tel: 86-532-8502-7355
Fax: 86-532-8502-7205

China - Shanghai
Tel: 86-21-5407-5533
Fax: 86-21-5407-5066

China - Shenyang
Tel: 86-24-2334-2829
Fax: 86-24-2334-2393

China - Shenzhen
Tel: 86-755-8864-2200
Fax: 86-755-8203-1760

China - Wuhan
Tel: 86-27-5980-5300
Fax: 86-27-5980-5118

China - Xian
Tel: 86-29-8833-7252
Fax: 86-29-8833-7256

ASIA/PACIFIC

China - Xiamen
Tel: 86-592-2388138
Fax: 86-592-2388130

China - Zhuhai
Tel: 86-756-3210040
Fax: 86-756-3210049

India - Bangalore
Tel: 91-80-3090-4444
Fax: 91-80-3090-4123

India - New Delhi
Tel: 91-11-4160-8631
Fax: 91-11-4160-8632

India - Pune
Tel: 91-20-3019-1500

Japan - Osaka
Tel: 81-6-6152-7160
Fax: 81-6-6152-9310

Japan - Tokyo
Tel: 81-3-6880-3770
Fax: 81-3-6880-3771

Korea - Daegu
Tel: 82-53-744-4301
Fax: 82-53-744-4302

Korea - Seoul
Tel: 82-2-554-7200
Fax: 82-2-558-5932 or
82-2-558-5934

Malaysia - Kuala Lumpur
Tel: 60-3-6201-9857
Fax: 60-3-6201-9859

Malaysia - Penang
Tel: 60-4-227-8870
Fax: 60-4-227-4068

Philippines - Manila
Tel: 63-2-634-9065
Fax: 63-2-634-9069

Singapore
Tel: 65-6334-8870
Fax: 65-6334-8850

Taiwan - Hsin Chu
Tel: 886-3-5778-366
Fax: 886-3-5770-955

Taiwan - Kaohsiung
Tel: 886-7-213-7828

Taiwan - Taipei
Tel: 886-2-2508-8600
Fax: 886-2-2508-0102

Thailand - Bangkok
Tel: 66-2-694-1351
Fax: 66-2-694-1350

EUROPE

Austria - Wels
Tel: 43-7242-2244-39
Fax: 43-7242-2244-393

Denmark - Copenhagen
Tel: 45-4450-2828
Fax: 45-4485-2829

France - Paris
Tel: 33-1-69-53-63-20
Fax: 33-1-69-30-90-79

Germany - Dusseldorf
Tel: 49-2129-3766400

Germany - Munich
Tel: 49-89-627-144-0
Fax: 49-89-627-144-44

Germany - Pforzheim
Tel: 49-7231-424750

Italy - Milan
Tel: 39-0331-742611
Fax: 39-0331-466781

Italy - Venice
Tel: 39-049-7625286

Netherlands - Drunen
Tel: 31-416-690399
Fax: 31-416-690340

Poland - Warsaw
Tel: 48-22-3325737

Spain - Madrid
Tel: 34-91-708-08-90
Fax: 34-91-708-08-91

Sweden - Stockholm
Tel: 46-8-5090-4654

UK - Wokingham
Tel: 44-118-921-5800
Fax: 44-118-921-5820

01/27/15